



GAYATRI VIDYA PARISHAD COLLEGE OF ENGINEERING
(Autonomous)

Madhurawada, Visakhapatnam

Affiliated to Andhra University, Visakhapatnam.

B.Tech I-Semester Regular & Supplementary Examinations February 2024

Basic Electrical and Electronics Engineering

[Common to Chemical, CSE, IT, CSE (Data Science) & CSE (AI&ML)]

Date: 13-02-2024


Time: 3 Hours

Max. Marks: 70


1. Answer ONE Question from each UNIT
2. All parts of a Question must be answered in one place to get valued.
3. All questions carry equal marks.

UNIT-I

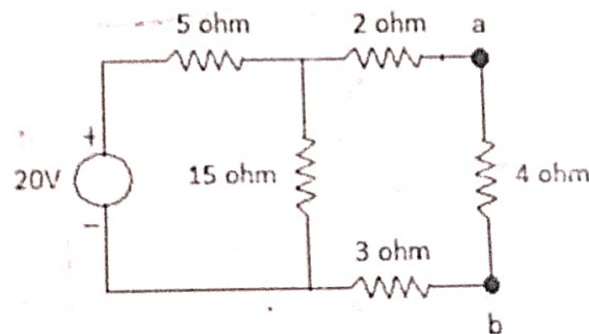- 1.a State the Kirchhoff's Laws and explain. 7 Marks
- b Find the current passing through 4 ohms resistance using Thevenin's Theorem. 7 Marks



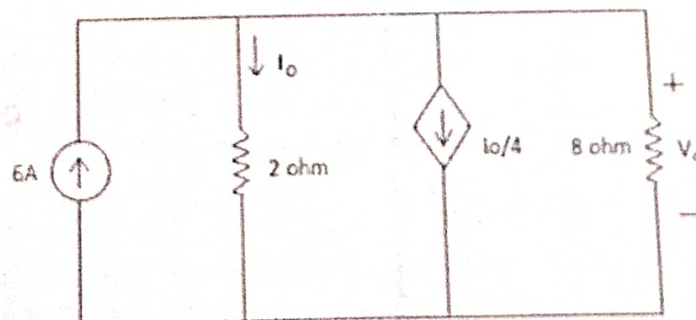- 2.a State and explain the Norton's Theorem. 7 Marks
- b Find V_0 and I_0 in the given circuit. 7 Marks



UNIT-II

- 2.a What is the need of a starter in DC motors? Briefly explain the working of 3-Point Starter. 7 Marks
- b A 6 pole DC generator is having 1200 lap connected armature conductors is producing an emf of 400 V in its armature winding. Find the speed of the generator if it is maintaining a flux of 10 mwb under each pole 7 Marks

- 4.a List the different types of DC generators and write down their voltage and current equations. 7 Marks
- b A DC Shunt motor absorbs a current of 19A from 220 V DC source. The armature and shunt field resistances are 1.5 and 225 ohms respectively. The total Iron and friction losses are 450 W. Find the efficiency of the motor. 7 Marks

UNIT-III

- 5.a Briefly discuss on the construction of Synchronous Generator. 7 Marks
- b In a 220/3000 Volt, 50 Hz Single Phase transformer, the maximum flux density is 2 wb/m^2 . The emf per turn is 10 V. Determine a) Number of primary and secondary turns b) cross sectional area of the core. 7 Marks
- 6.a Explain the Torque-Slip characteristics of a three-phase induction motor. 7 Marks
- b How do you conduct OC and SC tests on single phase transformer? Explain. 7 Marks

UNIT-IV

- 7.a Explain the Forward bias and Reverse bias characteristics of a PN junction diode. 7 Marks
- b What is MOSFET? Explain its operation. 7 Marks
- 8.a Explain the working of Full-Wave Rectifier with filter capacitor. Draw the input and output waveforms. 7 Marks
- b Explain, how the Zener diode acts as a voltage regulator. 7 Marks

UNIT-V

- 9.a Briefly, explain the characteristics and applications of an Op Amp. 7 Mark
- b Explain the Op Amp characteristics in Non-inverting configuration. 7 Mark
- 10.a Discuss on closed loop operation of an Inverting Op Amp. 7 Mark
- b Can an Op Amp be operated as a Voltage Follower? Explain. 7 Mark